

Lab 2: The Design Hierarchy

Frederick Meneses

January 22, 2023

Part I

1. If the truth table in Table 2.1 of the handout was given in full, how many rows would it have?

2^6 rows.

2. Export the schematic of the mux4to1 subcircuit as an image and include it in your report.

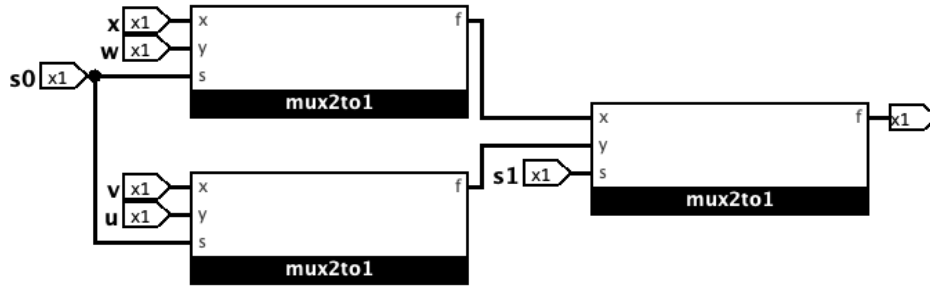


Figure 1: A schematic of the 4-to-1 multiplexer

Part II

1. Derive seven truth tables, one for each segment of the 7-segment decoder.

$D_{3:0}$	Character	S_0	S_1	S_2	S_3	S_4	S_5	S_6
0000	0	1	1	1	1	1	1	0
0001	1	0	1	1	0	0	0	0
0010	2	1	1	0	1	1	0	1
0011	3	1	1	1	1	0	0	1
0100	4	0	1	1	0	0	1	1
0101	5	1	0	1	1	0	1	1
0110	6	1	0	1	1	1	1	1
0111	7	1	1	1	0	0	0	0
1000	8	1	1	1	1	1	1	1
1001	9	1	1	1	1	0	1	1
1010	A	1	1	1	0	1	1	1
1011	b	0	0	1	1	1	1	1
1100	c	0	0	0	1	1	0	1
1101	d	0	1	1	1	1	0	1
1110	E	1	0	0	1	1	1	1
1111	F	1	0	0	0	1	1	1

2. Use Karnaugh maps to write seven Boolean functions for each segment so that they are optimized.

$$\begin{aligned}
S_0 &= \overline{v}x + \overline{u}w + \overline{u}vx + vw + u\overline{v}\overline{w} \\
S_1 &= \overline{u}\overline{v} + \overline{u}w\overline{x} + \overline{v}x + \overline{u}wx + u\overline{w}x \\
S_2 &= \overline{u}\overline{w} + \overline{u}x + \overline{w}x + \overline{u}v + u\overline{v} \\
S_3 &= \overline{u}\overline{v}x + \overline{u}w\overline{x} + \overline{v}wx + v\overline{w}x + u\overline{w} + uv\overline{x} \\
S_4 &= \overline{v}x + w\overline{x} + uw + uv \\
S_5 &= \overline{u}w\overline{x} + \overline{u}v\overline{w} + \overline{u}v\overline{x} + u\overline{v} + uw \\
S_6 &= \overline{v}w + v\overline{w} + v\overline{x} + u
\end{aligned}$$

3. Use the naming scheme HEX0, HEX1, ..., HEX6 for each subcircuit. Export each subcircuit schematic as an image and include it in your report.

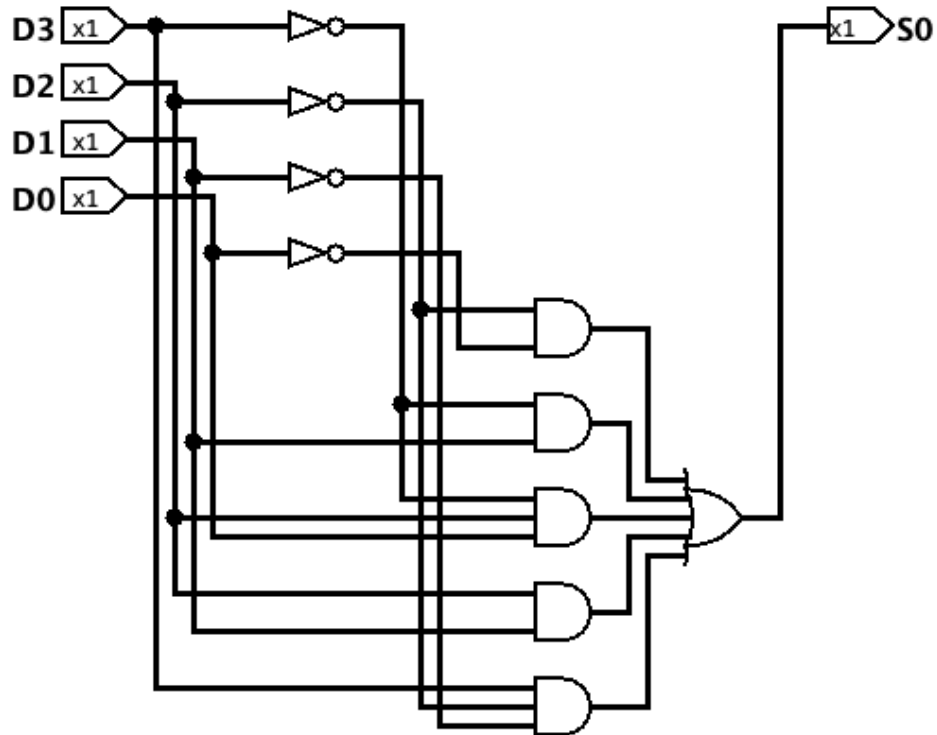


Figure 2: A schematic of HEX0

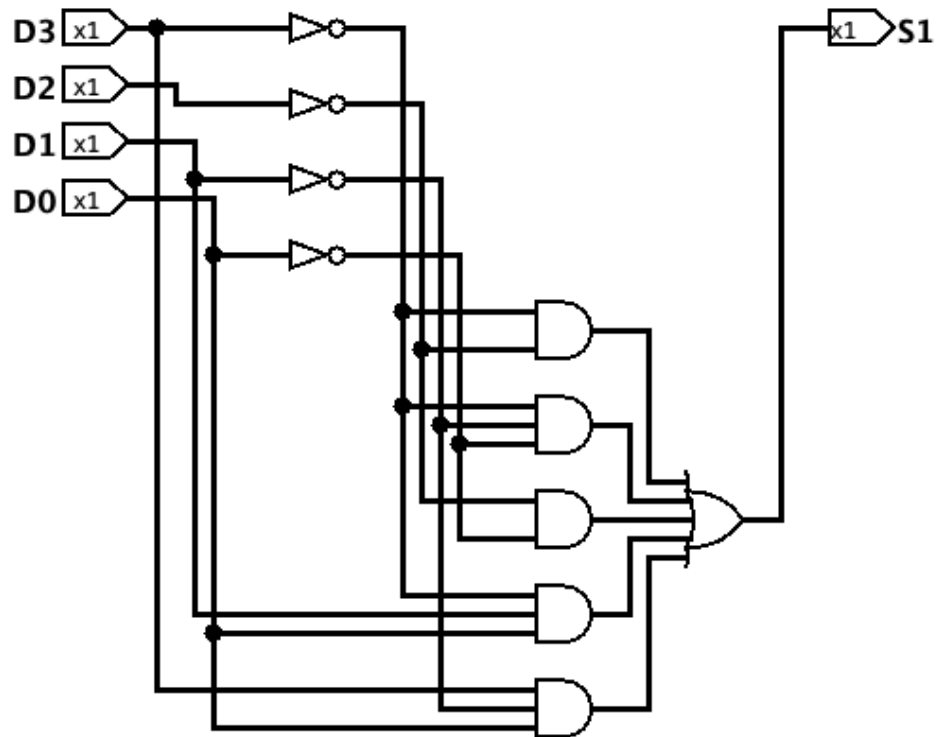


Figure 3: A schematic of HEX1

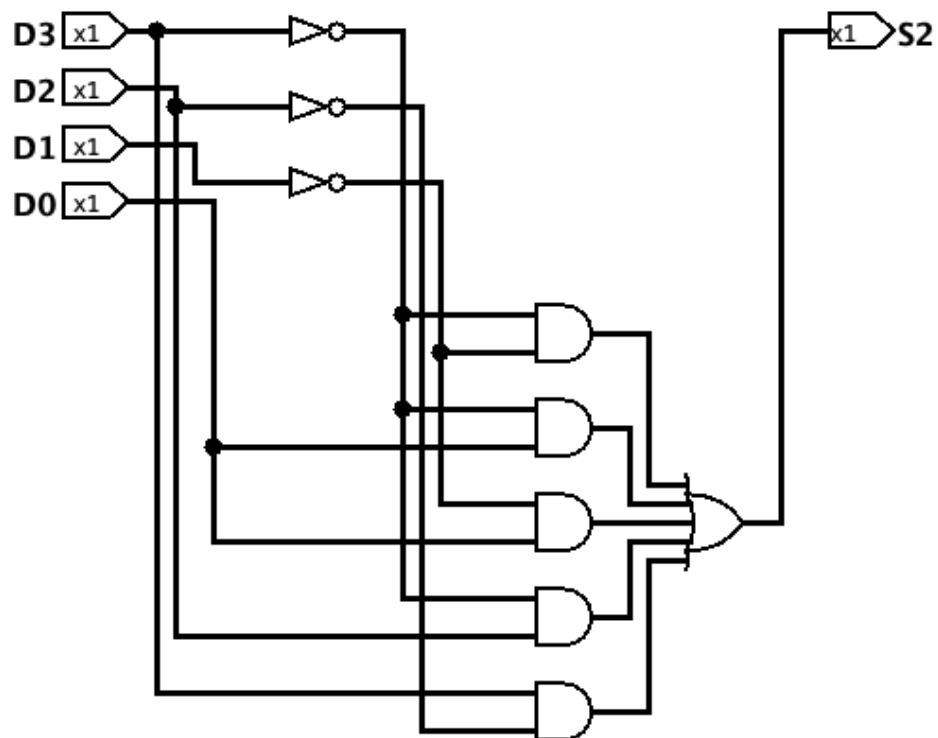


Figure 4: A schematic of HEX2

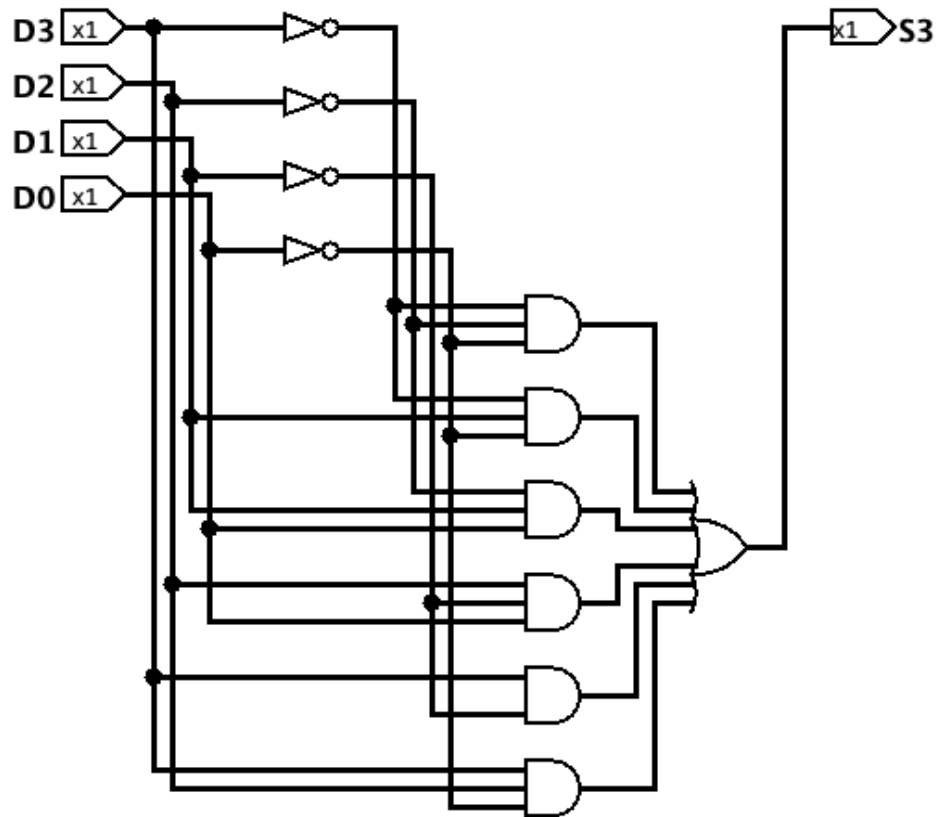


Figure 5: A schematic of HEX3

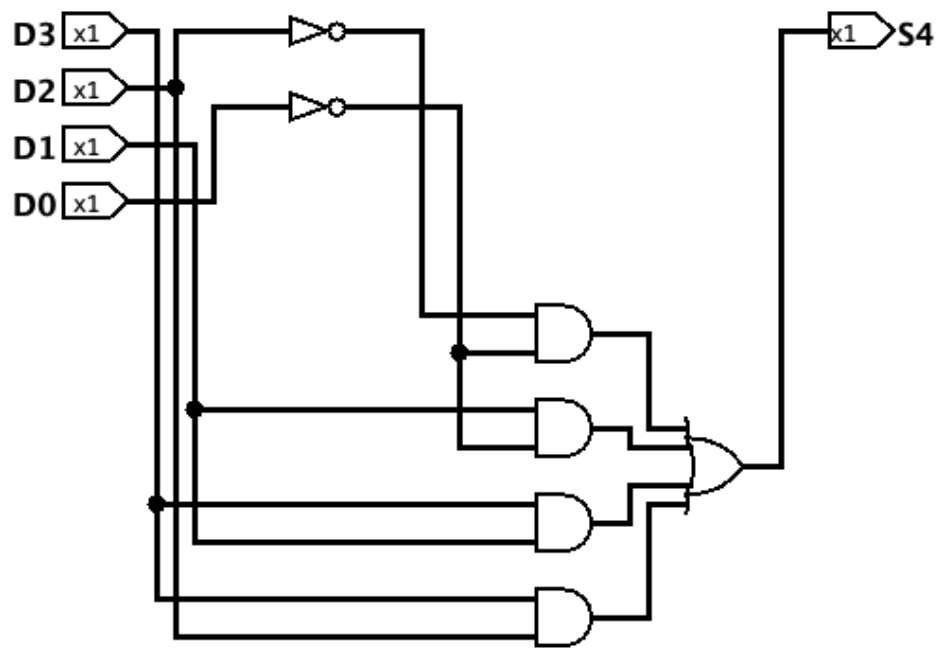


Figure 6: A schematic of HEX4

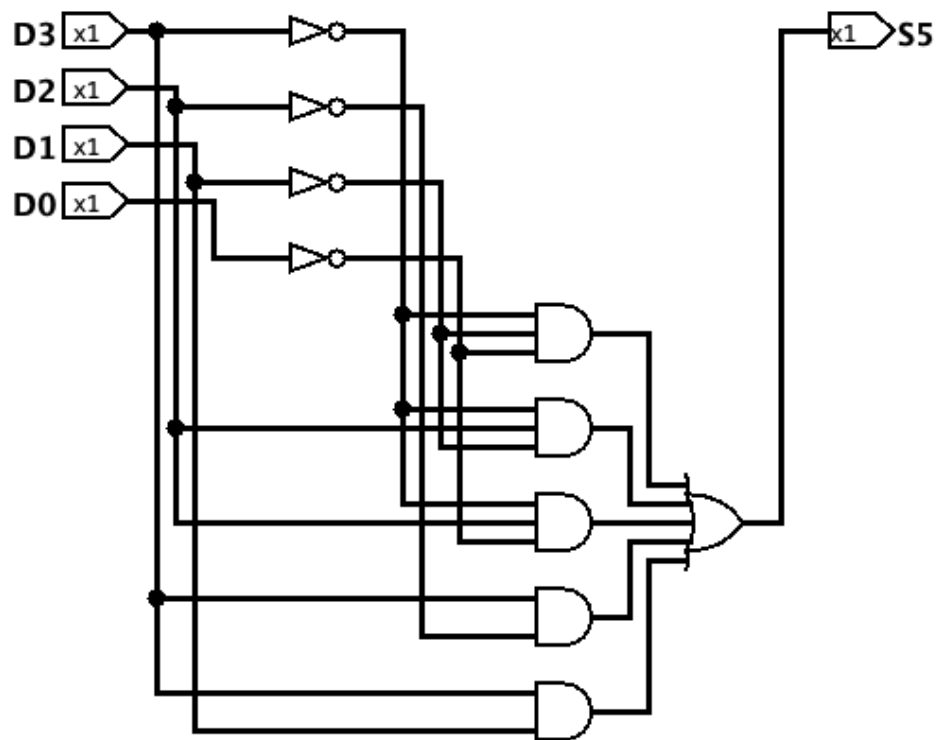


Figure 7: A schematic of HEX5

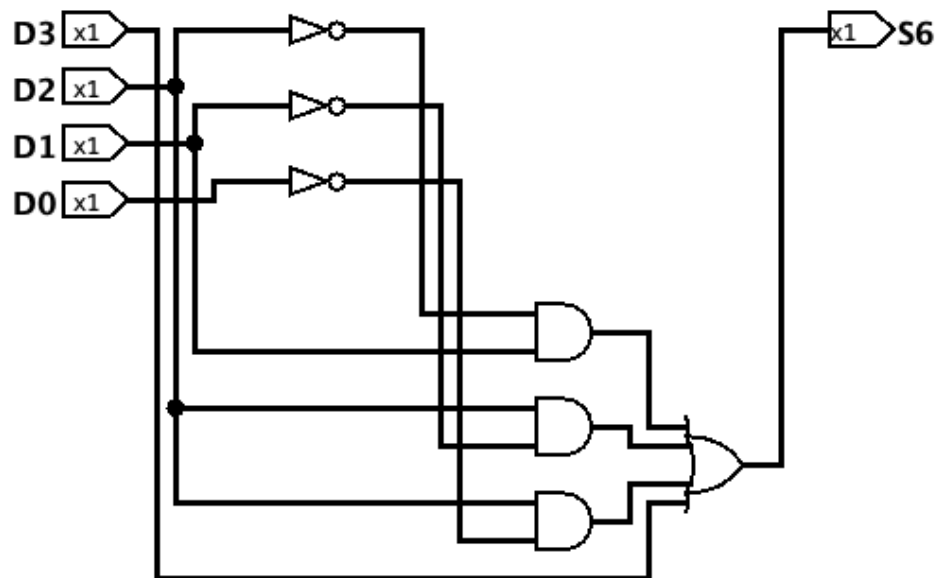


Figure 8: A schematic of HEX6