




Lab 7 Preparation

Lab 7 Components

- **Part I:** Create a memory unit
- **Part II:** Interface with the RGB Video
- **Part III:** RGB Video animation (bonus)

Part I: Memory Unit


- Creating a mini-RAM unit.
- Make use of the built-in **RAM**
 - Follow lab instructions to create a 4-bit RAM unit with 32 words.
 - Fill the RAM with values 0-F.
- Once completed, connect this RAM to the HEX display.

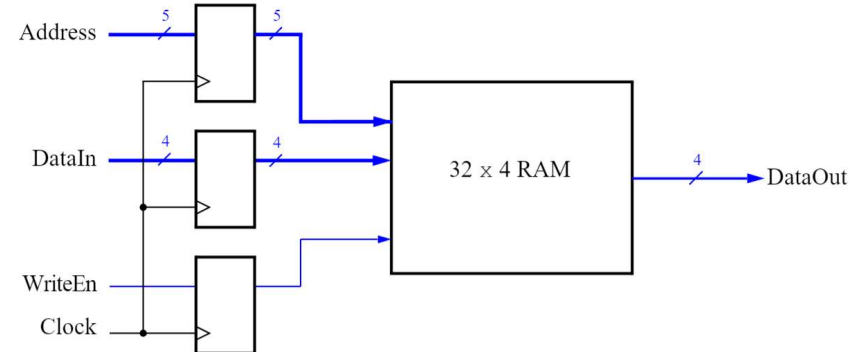

Part I: Read & Write Timing


- **Read:**

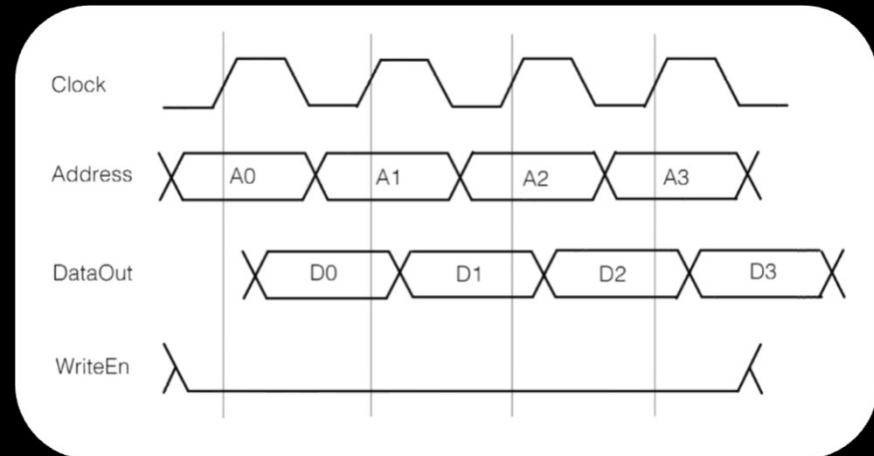- Note slight delay after clock signal, before data appears.




- **Write:**

- Note that only D1 and D2 are written (because of the WriteEn signal).

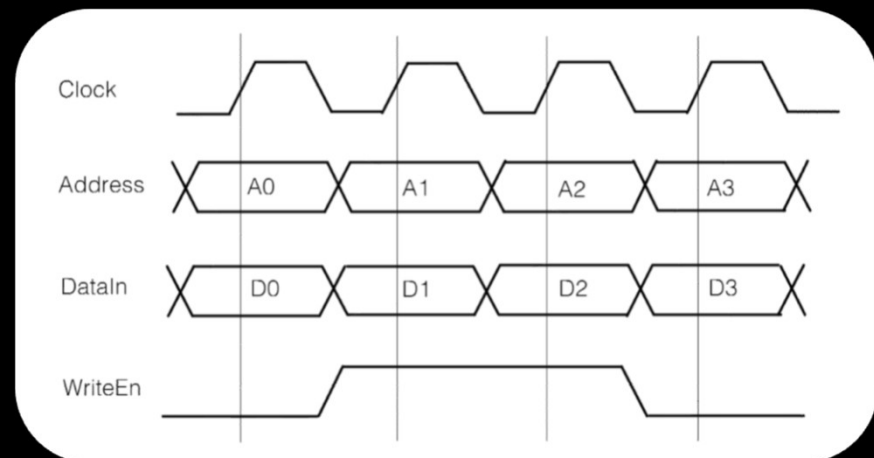


Part I: Filling memory

- Connect address register and data register to RAM.
- Fill all RAM locations with increasing values, starting at 0 at address 00000.
- Connect output to 7-segment display.

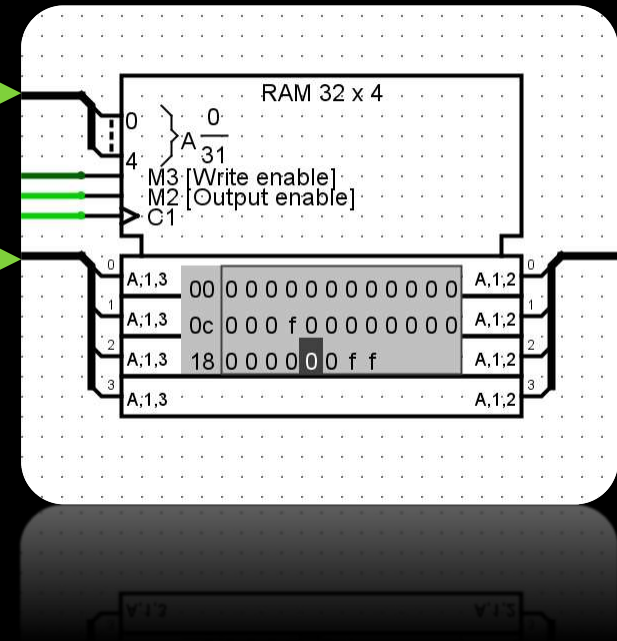


Part II: RGB Video

- The RGB Video component models the VGA display in the lab workstations.
- For this part, given input coordinates X and Y , draw a 16×16 box of coloured pixels, using X and Y as the top left corner of the box.

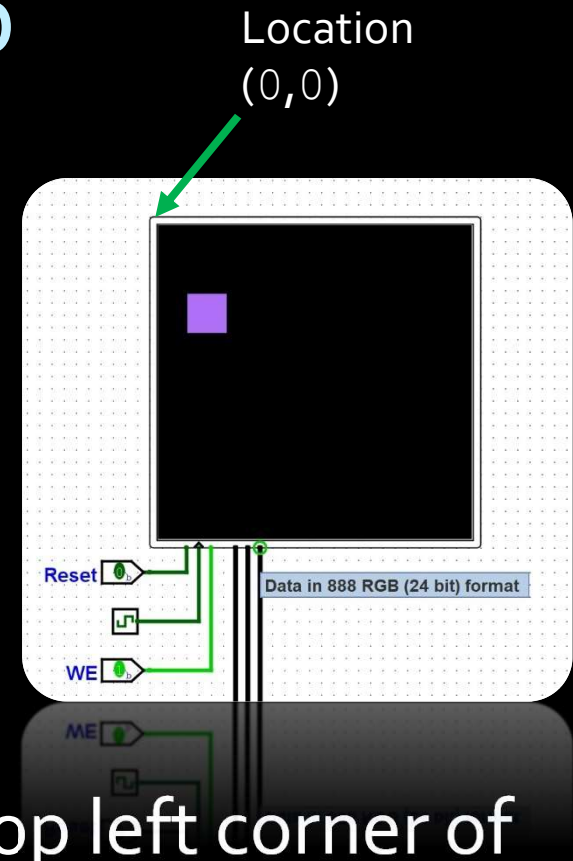


Part II: RGB Video

- The RGB Video component has 6 inputs:
 - **Reset**
 - **Clock**
 - **Write Enable**
 - Like lifting/dropping pen on paper.
 - **X Coordinate**
 - **Y Coordinate**
 - **Data in 888 RGB (24 bit) format**
 - Three sections of 8 bits, representing the RGB values for the pixel (see next slide for more detail)

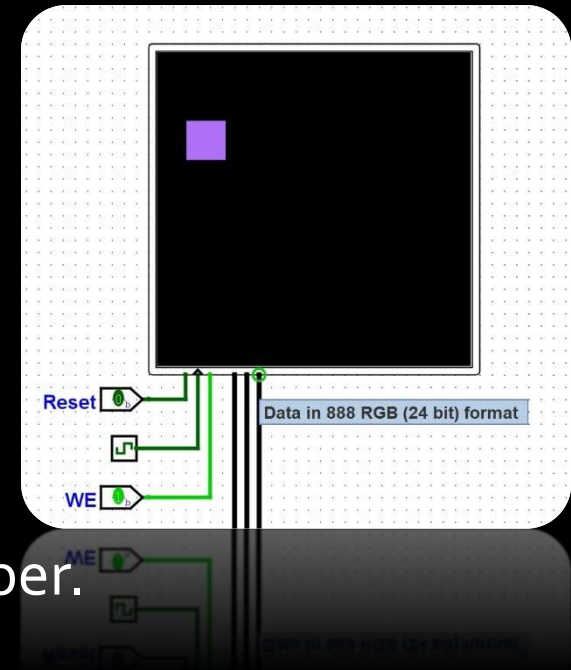

Part II: RGB Video

- Light colours are additive.
 - As opposed to paint, which is subtractive.
 - Light is made of red, green and blue components.
 - White light is the combination of all three.
- To create a colour, set the 8-bit values for the red, green and blue components and concatenate them into a 24-bit value.
 - Black = 0x000000, White = 0xFFFFFFFF

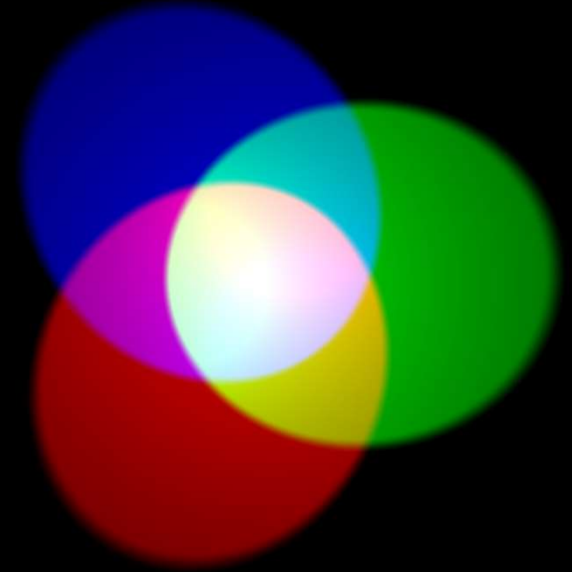

Part II: RGB Video

- Circuit components needed:
 - **RGB Video**
 - built into Logisim, check the handout for input details
 - **Datapath**
 - Takes in:
 - X and Y (through switches)
 - control signals (reset, clock, enable etc.)
 - **FSM:**
 - Controls datapath to load X and Y values, and iterate through the pixel locations that need to be updated (relative to X and Y).

Parts I & II: Hints

- Play around with the memory and RGB Video components to verify that they work.
 - E.g. Draw a single pixel on the RGB Video to start.
- The “datapath” doesn’t need to look like Lab 6.
 - Focus on the operations performed on X and Y .
- Consider using counters to store the offsets from X and Y that need to be displayed.
 - Maybe a single counter for both?
 - Counters can be part of your FSM as well.
- It’s Lab 7. You have full freedom to implement this however you like 😊

Part III: Animation (bonus)

- Note: This part is optional, but can be done for bonus marks in the course.
- Animate a box by drawing it, then waiting, then drawing another at a different location, then waiting...
- Many projects will use animation in some form, so you should try this part out!
 - Also...bonus marks! 😊

