




# Lab 4 Preparation

# What Lab 4 is about

- **Part I** (1 mark):
  - Implementing latches and flip-flops with IC chips
  - Last thing you'll do on the breadboards!
- **Part II** (1 mark):
  - Using a register to store & provide ALU values
    - Register stores the output of the ALU
    - Same register also provides an input to the ALU
- **Part III** (1 mark):
  - Implement a shift register.

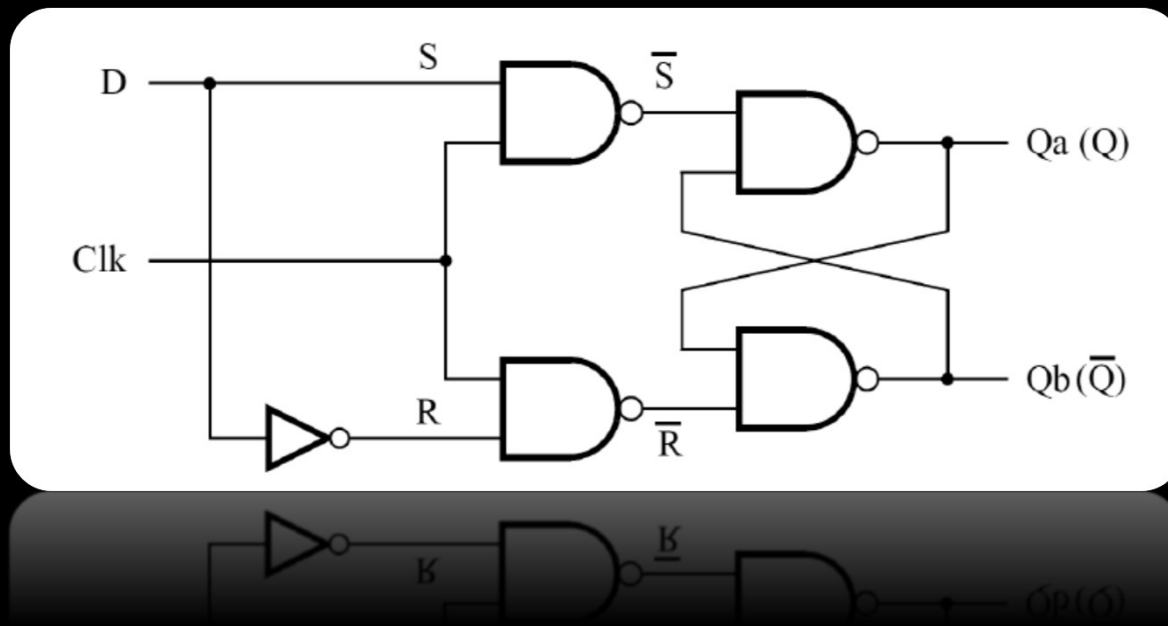
# Lab 4 - Part I

- Create a D latch on the breadboard!
  - ▣ Using NAND gates!
- Same procedure as for Lab 1:
  - ▣ Use Logisim to design a circuit with IC chips
  - ▣ Test your circuit using the Poke tool.


 
# Lab 4 – Part I


- ...then, create a D flip-flop out of D latches ☺



- How are you going to test this?
  - Logisim test vectors have difficulty here ☺
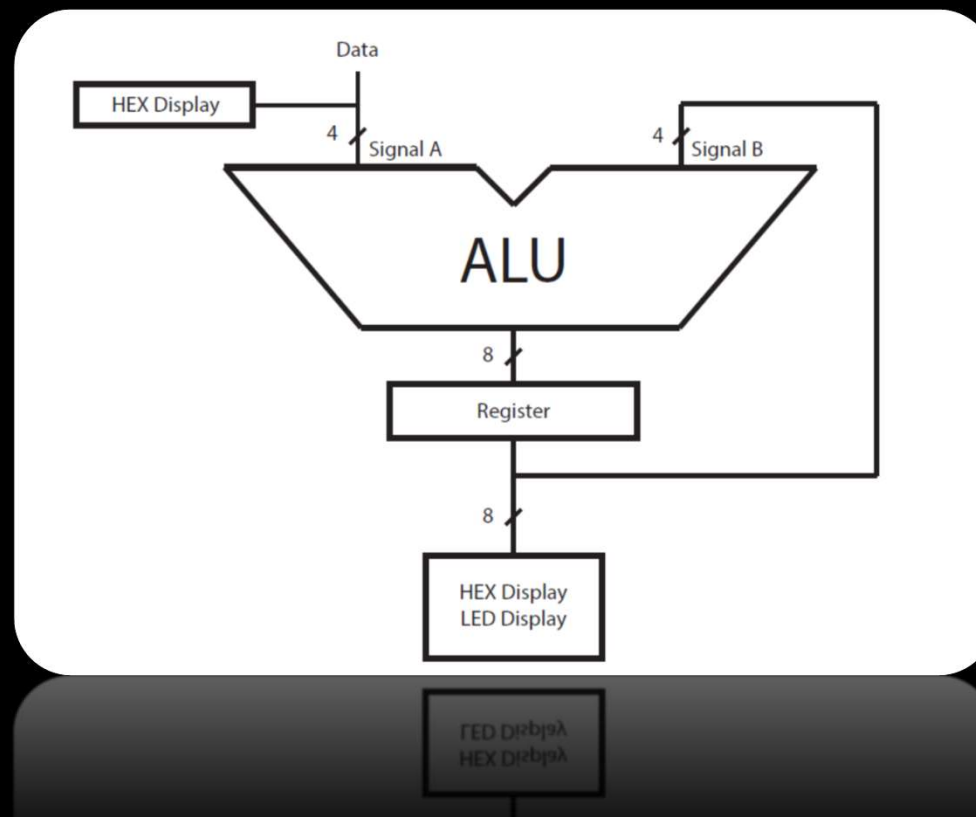
# Lab 4 – Part II

- Enhance the ALU from last week:
  - More operations (e.g. multiplication, shifting)
  - Store the result in a register.



# Lab 4 – Part II


- Old operations:

- 0 :  $A+1$  (using your adder)
- 1 :  $A+B$  (using your adder)
- 2 :  $A+B$  (using the Logisim adder)
- 3 :  $A \text{ XOR } B$  in lower four bits,  $A \text{ OR } B$  in upper four bits
- 4 : Reduction OR operation on A & B

- New operations:

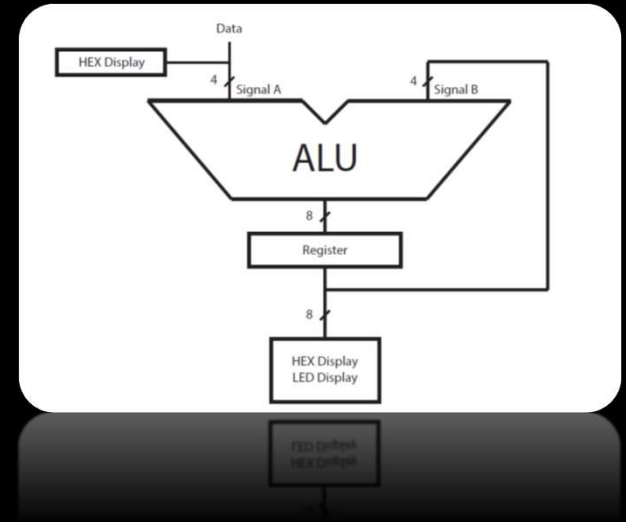- 5 : Left shift B by A bits
- 6 : Logical right shift B by A bits
- 7 :  $A \times B$  (multiplication)

} All of these are supplied through the collection of components in Logisim.



# What does it mean to shift?

- Suppose that  $B = 00010110$  and  $A = 00000011$
- “Left shift B by A bits” = shift every bit in B three bits to the left (since  $A = 3$ ).
  - One bit to the left:  $B \rightarrow 00101100$
  - Two bits to the left:  $B \rightarrow 01011000$
  - Three bits to the left:  $B \rightarrow 10110000$
- One bit gets shifted off the left side each time, and a zero is shifted into the right.

# Logic vs Arithmetic Shift

- Function 6 of the ALU is a **logical right shift**.
  - This is the same as the left shift, but to the right.
- What does the word “logical” signify?
  - B is storing binary values, but not a number.
  - When shifting right, shift in zeroes on the left side.
- What if B is storing a binary number?
  - Then you perform an **arithmetic right shift**.



# Logic vs Arithmetic Shift



- Arithmetic right shifts **replicate the sign bit** instead of using zero to fill in the most-significant bit(s).
  - Used when shifting signed numbers.
  - For unsigned numbers, use logical shift (like in Part 2).
- Example: Shift 10010000 right by 3 bits
  - Arithmetic → **111**10010
  - Logical → **000**10010

# Logic vs Arithmetic Shift

- Why do we shift in the sign bit?
- Shifting B left A bits multiplies B by  $2^A$ .
  - Again, assuming that  $B = 00010110$  ( $22_{10}$ )
  - If  $A=1$ ,  $B \rightarrow 00101100$  ( $44_{10}$ )
  - If  $A=2$ ,  $B \rightarrow 01011000$  ( $88_{10}$ )
- Shifting B right A bits divides B by  $2^A$ , but only if you preserve the sign bit!
  - Suppose that  $B = 11110110$  ( $-10_{10}$ )
  - Arithmetic shift right:  $B \rightarrow 11111011$  ( $-5_{10}$ )
  - Logical shift right:  $B \rightarrow 01111011$  ( $123_{10}$ )

  
# Logisim Shifter Components

- Getting back to Lab 4, part II...
- Shifter components can be found in Logisim under Arithmetic > Shifter.
  - You can change the shift type in Properties.
  - More details can be found at:
    - <http://www.cburch.com/logisim/docs/2.3.0/libs/arith/shifter.html>
- Illustrated below: Logical Shift (left and right)



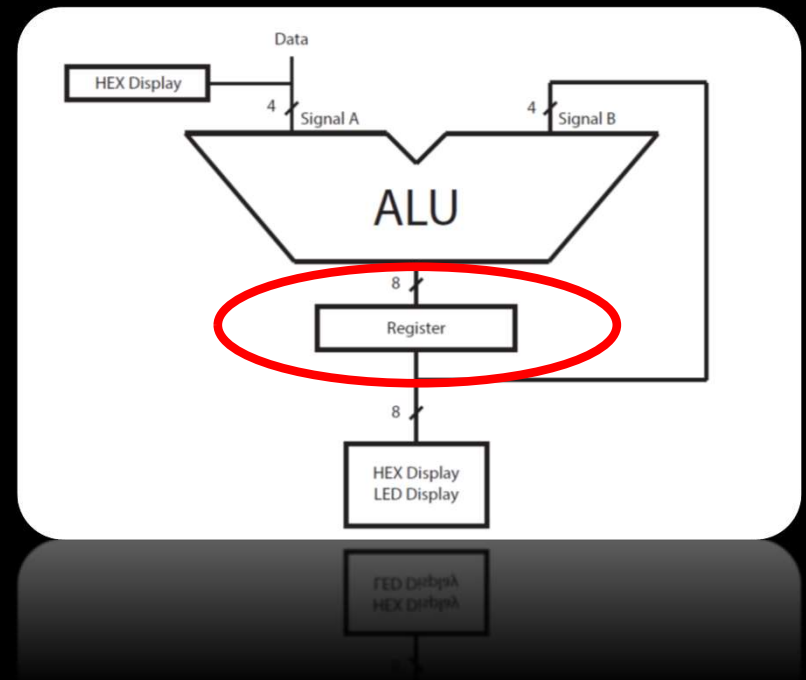
# Lab 4 – Part II

- The other major addition to the ALU is the **register** that stores the output value.
  - 8 bits (flip-flops) long.
  - Component found in Memory > Register.
  - You can change the number of flip-flops in Properties > Data bits.


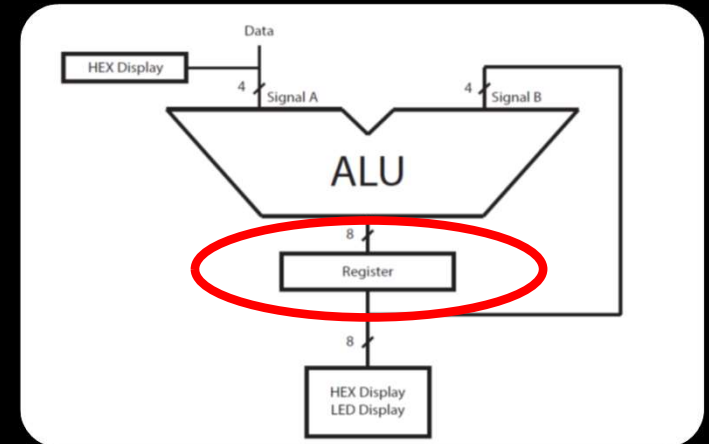
# Why is the register here?

- The ALU is a **transparent** device, meaning that input values are passed straight through to the output (with some small delay).
  - Since the output of the ALU feeds back to input B, without the register the ALU output would change constantly.
  - The register has a **clock signal** that only updates its contents when the clock changes from 0 to 1.



# Final notes about Part II

- Make sure that for addition operations, the output preserves the carry bit.
  - For example, if  $A=1101$  and  $B=1011$ , the ALU output should be  $00011000$ .
  - If you didn't do this for Lab 3, make sure to do it for Lab 4 😊
- The input B to the ALU is the least significant bits of the ALU output.
- Remember to display the inputs and outputs on seven-segment displays (and outputs on LEDR)


# Lab 4 – Part III

- Make an 8-bit shift register out of 8 individual shifter units (each unit stores a single bit)
  - Similar to how the ripple carry adder was created.
- Below: the diagram for a single shifter unit.

**load\_val**: external value to load into register.

**in**: input value coming from next shifter unit

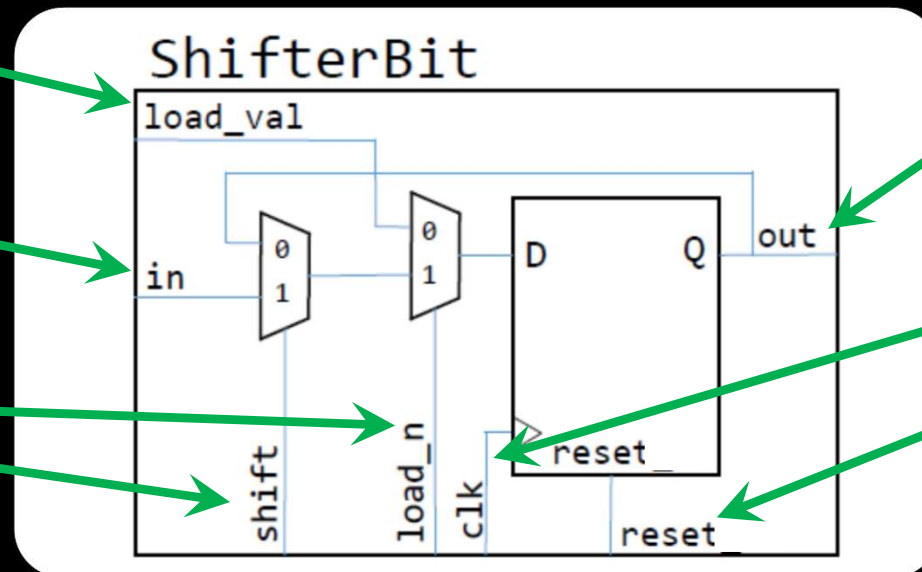**shift, load\_n**: are we doing a shift or load operation?




**out**: outputs the contents of this shifter unit.

**clk**: external clock signal for register.

**reset**: clear unit contents to zero.
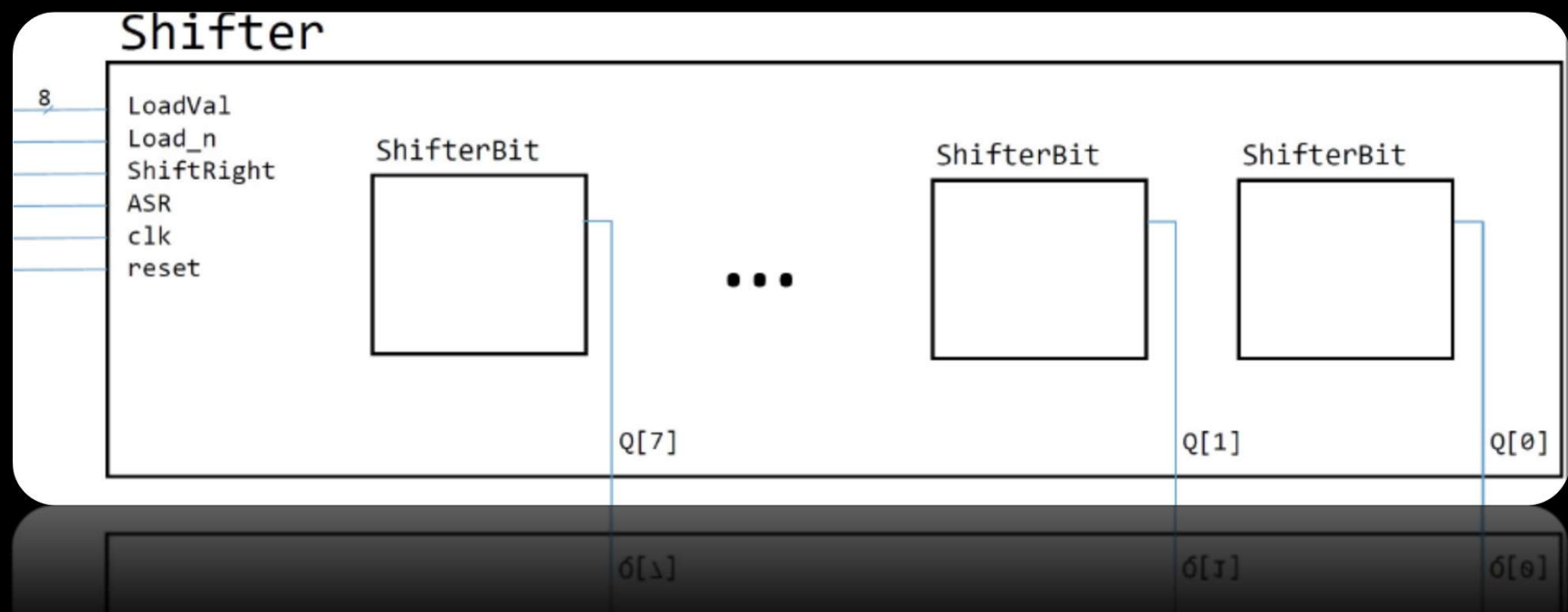
# Lab 4 – Part III

- Once you've made a module for the shifter unit, connect 8 shifter units together to make the **shift register**.
- Note:
  - This shift register only shifts to the right.
  - The shift register can load a new value from the 8 input bits in LoadVal (only happens when Load\_n is **low**)





# Lab 4 – Part III

- Shifter signals:
  - `Load_n` signals the ShifterBit units to load a new value from the `LoadVal` input (that you provide)
  - `clk` (the clock signal) signals when the ShifterBit contents should change (both shifting and loading operations).
  - `reset` is asynchronous (independent of the `clk` signal).
  - `ShiftRight` tells you to shift, `ASR` tells you what kind of shift to do (0=logical, 1=arithmetic).

